

Complex Example

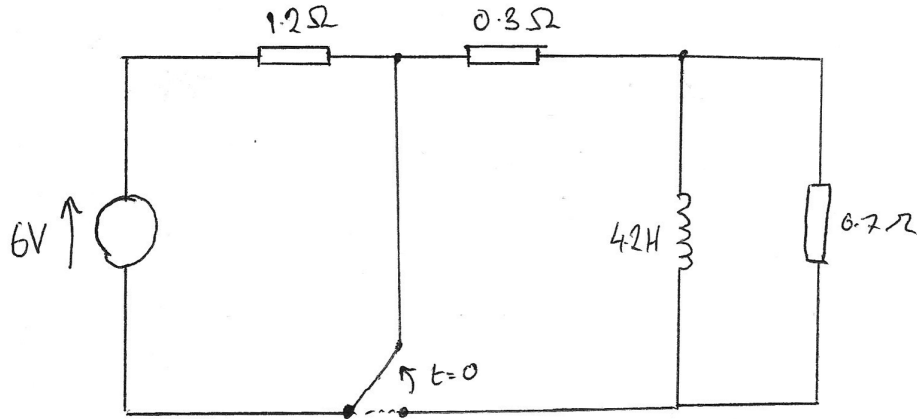


Figure 1: A Circuit Diagram for Analysis

After being in position A for a long time the switch moves to position B > at $t = 0$.

Derive an equation for the current i_L through the inductor for $t > 0$.

Because the question says “after a long time” this means that current and voltages will be constant, so we start by working out the current just before the switch is toggled.

At DC the inductor will act as a short circuit, so the 0.7Ω resistor is shorted out, meaning the circuit before $t = 0$ is effectively a circuit with only a power source and two resistors.

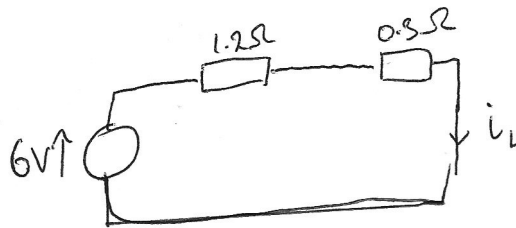


Figure 2: Equivalent circuit before $t = 0$

So you can easily calculate the current here using Ohm’s Law.

$$i_L = \frac{V}{R} = \frac{6}{0.3 + 1.2} = 4A$$

And because the current in an inductor cannot change instantly we then know that

$$i_L(0) = 4A$$

Now, after $t = 0$ the circuit can be described as this

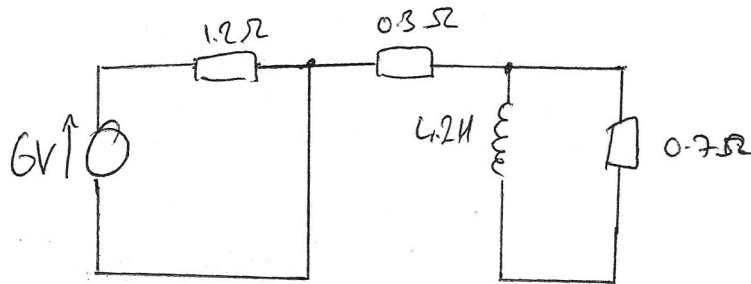


Figure 3: Equivalent circuit after $t = 0$

Because there is only one connection between loops A and B, there is not interaction between them, so for us we only need to consider loop B, and inductor discharging over a resistor, an RL Circuit.

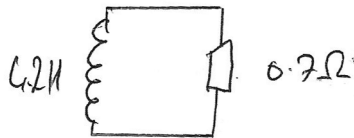


Figure 4: RL Circuit

Which has the solution

$$i_L(t) = I_0 e^{-\frac{R}{L}t}$$

$$i_L(t) = I_0 e^{-\frac{0.7}{4.2}t}$$

Which simplifies, and using the initial condition from earlier

$$i_L(t) = 4e^{-6t}$$