

## Sinusoidal Sources

You can introduce a sinusoidal source into a circuit, with  $V = V_0 \sin \omega t$ . The Fourier series says that you can decompose any signal into the sum of sine waves. The response to single sine waves is called AC theory.

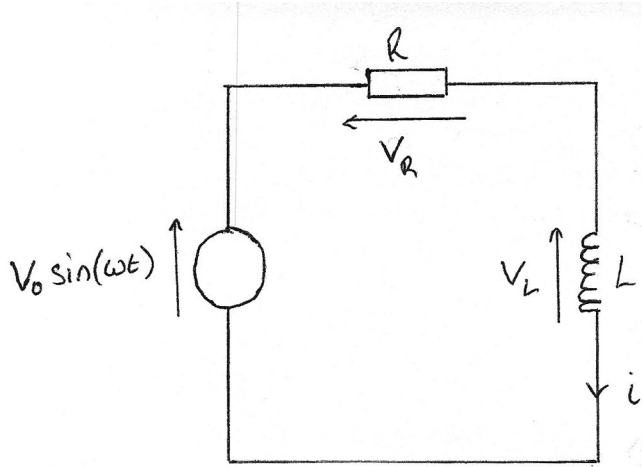


Figure 1: An LC Circuit with a Sinusoidal Source.

**KVL:**  $V_0 \sin(\omega t) - V_R - V_L = 0$

**KCL:** One loop therefore one current  $i$

A combination with the ideal relations gives

$$\frac{di}{dt} + \frac{R}{L}i = \frac{V_0}{L} \sin(\omega t)$$

To which we can guess a solution

Guess

$$i(t) = I_0 \sin(\omega t + \phi)$$

Differentiate

$$\frac{di}{dt} = I_0 \omega \cos(\omega t + \phi)$$

Substitute

$$I_0\omega \cos(\omega t + \phi) + \frac{R}{L}I_0 \sin(\omega t + \phi) = \frac{V_0}{L} \sin(\omega t)$$

To verify that this is correct we need to find values of  $(I_0, \phi)$  that work for  $t \geq 0$ .

So, for  $t = 0$

$$0 = I_0\omega \cos(\phi) + \frac{R}{L} \sin(\phi)$$

Factorising  $I_0$

$$\omega \cos(\phi) + \frac{R}{L} \sin(\phi) = 0$$

Then, dividing through by  $\cos(\phi)$

$$\omega + \frac{R}{L} \tan(\phi) = 0$$

So, for our guess to be correct

$$\phi = \tan^{-1} \left( -\frac{\omega L}{R} \right)$$

Then, you can do the same for  $t = \frac{\pi}{2\omega}$ . You use this value because it shifts a sine function into the cosine function, and the cosine function to the negative of the sine function.

$$I_0\omega \cos(\omega t + \phi) + \frac{R}{L}I_0 \sin(\omega t + \phi) = \frac{V_0}{L} \sin(\omega t)$$

$$\frac{V_0}{L} \sin \left( \frac{\pi}{2} \right) = I_0 \cos \left( \frac{\pi}{2} + \phi \right) + \frac{R}{L}I_0 \sin \left( \frac{\pi}{2} + \phi \right)$$

$$\frac{V_0}{L} = -I_0 \sin(\phi) + \frac{R}{L}I_0 \cos(\phi)$$

Now, using trigonometric identities you can find a nicer expression for substitution, using our known value for  $\phi$ .

$$\sin \phi = \frac{-\omega L}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\cos \phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

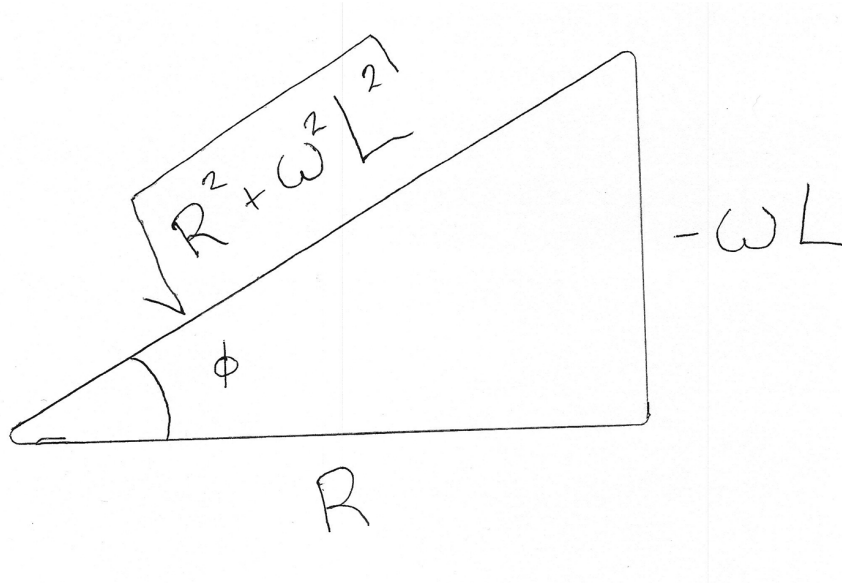


Figure 2: Diagram representing  $\tan \phi$  as a triangle.

Then, by substitution

$$\frac{V_0}{L} = -I_0\omega\left(\frac{-\omega L}{\sqrt{R^2 + \omega^2 L^2}}\right) + I_0\frac{R}{L}\left(\frac{R}{\sqrt{R^2 + \omega^2 L^2}}\right)$$

$$\frac{V_0}{L} = \frac{I_0}{L} \frac{R^2 + \omega^2 L^2}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\frac{V_0}{L} = \frac{I_0}{L} \sqrt{R^2 + \omega^2 L^2}$$

$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

If the guess is correct then our equations for  $I_0$  and  $\phi$  are correct. So finally we have to verify our solution by a final substitution back into  $i(t)$

$$i(t) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$